



As you can see the circuit has an input for the signal and two outputs which can be used to split the signal between two different appliances, (i.e. two line amplifiers, a monitor amplifier and a small amplifier etc.) Connected as it is shown in the diagram a 1126 with a 1127 form a complete compact microphone preamplifier with tone controls and master volume.

